



Politecnico di Torino

Microelectronic Systems

DLX Microprocessor: Design & Development

Final Project Report

Master degree in Electronics Engineering

Authors: group_19

Castagno Fabio - s242018
Rossi Luca - s239951

Referents: Prof. Mariagrazia Graziano, Giovanna Turvani

October 30, 2017

Contents

1	Summary	1
2	DLX	2
3	Control Unit	5
3.1	Control Word	5
3.2	R-type instruction	6
3.3	J-type instruction	6
3.4	I-type instruction	7
3.5	Branch and Jump management	7
4	Data Path	9
4.1	Fetch	9
4.2	Decode	9
4.2.1	Register file	10
4.3	Execute	10
4.3.1	ADDER	11
4.3.2	COMPARATOR	12
4.3.3	MULTIPLIER	13
4.3.4	Shifter	14
4.3.5	Logic unit	14
4.4	Memory	15
4.5	Write back	15
5	Simulation	16
5.1	Register file	16
5.2	Generic program test	16
6	Synthesis	18
6.1	ALU synthesis	18
6.2	DLX synthesis	21
7	Place & Routing	24
A	Instructions	25
A.1	Instruction set	25
B	Datapath	26
B.1	Structure	26
C	VHDL	27
C.1	SparseTreeCarryGenN	27
C.2	bidir_shift_rot_N_logic	29
C.3	bidir_shift_rot_N	32
D	SCRIPTS AND PROGRAMS	34
D.1	Final simulation script	34
D.2	4x4 matrix multiplication	36

CHAPTER 1

Summary

The project consists in the design, simulation and synthesis of a 5 stage pipelined DLX processor core in VHDL. After the basic functionalities it implements also: an extended ISA and an advanced ALU. Everything was optimized for delay and power efficiency. Physically implementation with place, route and clock tree synthesis. Our choice is to make the PRO version of the DLX, with some features added as:

- expanded ISA
- data-path optimization
- hazard control (some particular cases)
- static branch prediction

CHAPTER 2

DLX

The DLX has a RISC architecture (Reduced Set Instruction Computer). The block diagram is shown in figure 2.1. It uses 32 integer general purpose registers and 32 floating point registers. In this typical architecture there are two different memories, one for the instructions and one for data.

 


Figure 2.1: General schematic of a microprocessor based system

It uses only 2 addressing modes:

- **Immediate**: the content of a register is added to a value and the result is stored back
- **Displacement**: the content of a register is added to the content of memory at one specific address

The main structure of the system is composed by:

- **Program Counter**: register that always points the next instruction cell memory
- **Instruction register**: register that contains the instruction to be executed
- **Control Unit**: coordinates all the necessary actions in order to execute the stream of instructions
- **Data Path**: collection of units that are able to perform the data processing operations, it typically contains adders, multiplier, registers ecc.

The DLX datapath structure is shown in the following image 2.2. From this starting point we make our customized version.

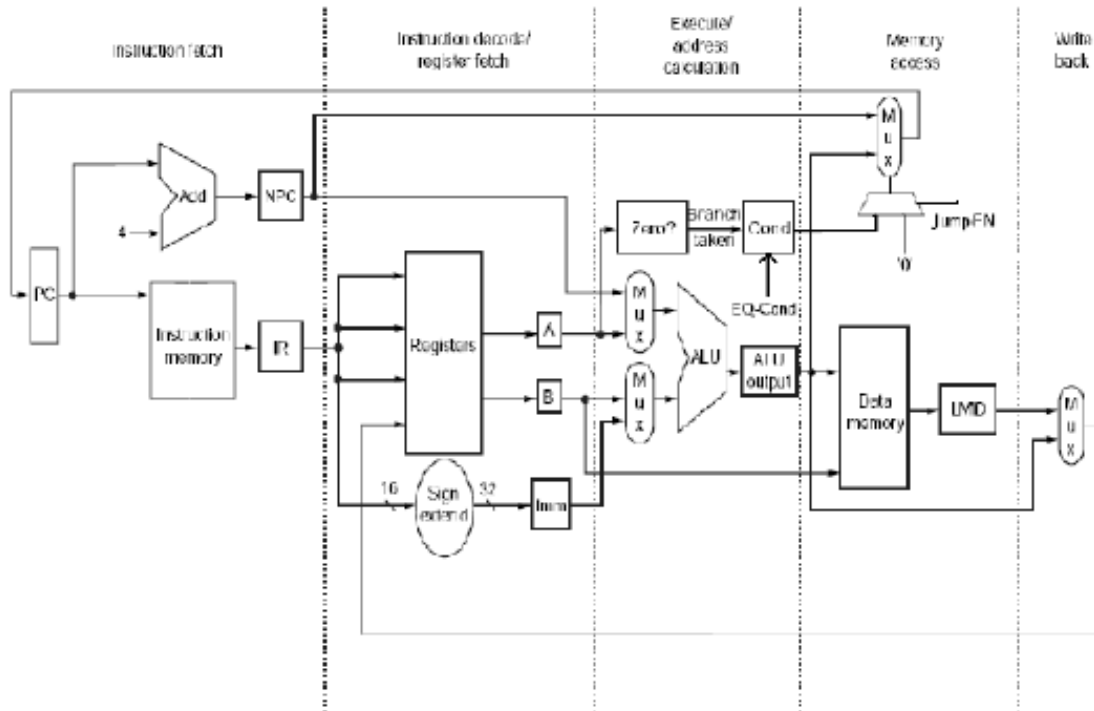


Figure 2.2: DLX datapath

There are 3 types of instructions (I - R - J) all 32 bits width with a 6-bit primary opcode.

- **I-type:** normally they are load and store instructions, operations with immediates or conditional branches
- **R-type:** they are ALU register to register operations
- **J-type:** they are jump, trap or return from exception

Every DLX instruction is implemented in at most five clock cycles:

IF ID EX MEM WB

- **Instruction fetch (IF) cycle:** Sends out the PC and fetches the instructions from memory into the instruction register (IR) and increments the PC by 4 to address the next one.
- **Instruction decode/register fetch (ID) cycle:** Decodes the instruction and accesses the register file (RF) to read the registers. Decoding is done in parallel with reading registers, which is possible because these fields are at a fixed location in the DLX instruction format. This technique is known as fixed-field decoding.
- **Execution/effective address cycle (EX):** The ALU operates on the operands (A or B/Imm or both) prepared in the previous cycle and the result is stored in a register.
- **Memory access/branch completion (MEM) cycle:** Accesses memory if needed. If instruction is a load, the data returned by the memory is placed in a register. Otherwise if it is a store, the data from the register is written into memory. In both cases the address used is the one computed in the prior cycle.
- **Write-back(WB) cycle:** Writes the result into the register file, whether it comes from the memory system or from ALU.

The processor is fully pipelined, this approach exploits parallelism and is based on concurrently perform different phases of processing. The general assumption is that the phases are independent between different operations and can be overlapped. If this condition is not respected the processor stalls the downstream phases. So multiple operations can be processes simultaneously for every different phase. The following timing diagram shows how it works:

Instruction cycle	1	2	3	4	5	6	7	8
i	IF	ID	EX	MEM	WB			
i+1		IF	ID	EX	MEM	WB		
i+2			IF	ID	EX	MEM	WB	
i+3				IF	ID	EX	MEM	WB
i+4					IF	ID	EX	MEM

Figure 2.3: Pipeline timing

With this approach we must pay attention to some problems that can occur, for example hazards. There are some techniques that try to prevent hazards.

CHAPTER 3

Control Unit

The top entity of our DLX is composed of two macroblocks, the hardwired CU and the datapath. The main reason that brings us to choose an hardwired Control Unit implementation instead of a Microprogram one is the high speed of this kind of architecture. The main drawback is the lower flexibility and possibility to manage complex instructions. The implementation is made through use of combinational logic units, featuring a finite number of gates that are able to generate the results that we need according to the instruction that we provide. It can be seen as a big look-up table. The CU receives the instruction word and two signals, clock and reset. The aim of the CU is to take these informations, elaborate them and produce the right control signals to the datapath. In order to delay the execution of each stage (pipeline), flip-flops are added.

3.1 Control Word

The control word size is 42 bits and each instruction has its own unique configuration. In Appendix A are reported all the instructions that our DLX is able to handle. In the following is shown the exact composition of the control word and the function of every single bit that compose it.

Listing 3.1: Control Word

```
1  — FETCH stage signals
   FS_Rst          <= CWSF(41); — reset to fetch stage
3   FATCH.En       <= CWSF(40); — enables the fetch stage registers
   FATCHRstMux21_Sel <= CWSF(39); — 1 reset of the stage if branch or jump 0
   FS_Rst
5   PCMux41_Sel    <= CWSF(38 downto 37); — 1 1 Beqz 10 Bneqz 01 Jump 00 '0'
   IRAM_Rst        <= CWSF(36); — reset of IRAM
7
9  — DECODE stage signals
   DECODE.En       <= CWSF(35); — enables the decode stage registers
   DECODE_Rst      <= CWSF(34); — reset the decode stage registers
11  RF_Rst         <= CWSF(33); — reset the register file
   RF_RD1          <= CWSF(32); — read on port 1 of register file
13  RF_RD2         <= CWSF(31); — read on port 2 of register file
   R1Mux21A_Sel    <= CWSF(30); — (1 AddrR1=R0 0 AddrR1=AddrR1)
15  R2Mux21B_Sel    <= CWSF(29); — (1 AddrR2=R0 0 AddrR2=AddrR2)
   RWMux41WR_Sel   <= CWSF(28 downto 27); — (11 AddrWR=R31 10 AddrWR=R0 01
   AddrWR=AddrR2 00 AddrWR=AddrR3)
17  ImmMux21_Sel    <= CWSF(26); — (1 Imm26 0 Imm16)
19
21 — EXECUTE stage signals
   EXECUTE.En      <= CWSE(25); — enables the execute stage registers
   EXECUTE_Rst     <= CWSE(24); — resets the execute stage registers
   OPBMux41_Sel    <= CWSE(23 downto 22); — (11=4 10=0 01=Imm 00=B)
23  OPAMux21_Sel    <= CWSE(21); — (1=PC.ret 0=A)
   ALU_Sel         <= CWSE(20 downto 17); — selection signals for the ALU
   operation
25  ALU_Unsign      <= CWSE(16); — execute an unsigned operation in the ALU
   ALU_Arith_logN   <= CWSE(15); — (1 arithmetic shift 0 logical shift)
27  StatusMux81_Sel <= CWSE(14 downto 12); — select the flag of the ALU that we
   want to propagate
29
31 — MEMORY stage signals
   MEMORY.En       <= CWSM(11); — enables the memory stage registers
   MEMORY_Rst      <= CWSM(10); — reset the memory stage registers
   DATAMEM.En      <= CWSM(9); — enables the data memory
33  DATAMEM_Rst     <= CWSM(8); — reset the data memory
   DATAMEM_Read_Wrn <= CWSM(7); — (1 read from the memory 0 write to the memory)
35  DATAMEM_Word     <= CWSM(6); — parallelism of the memory operation is 32 bit
   DATAMEM_HalfWord <= CWSM(5); — parallelism of the memory operation is 16 bit
37  DATAMEM_Byte     <= CWSM(4); — parallelism of the memory operation is 8 bit
   DATAMEM_Unsign   <= CWSM(3); — the number that we want store or read is
   unsigned
```

```

39  — WRITE BACK stage signals
41  RF_WR      <= CWSWB(2);
    WBMux41_Sel <= CWSWB(1 downto 0); — (11=Memory_data 10=ALU_data 01=
    Status_data 00='0')

```

During the rising edge of the clock, the control word for the current instruction is determined through a process, while on the falling edge, it is sent to the chain of registers that performs the pipeline. The three different kind of instructions will be treated separately but the way we handle them is similar.

3.2 R-type instruction

They are ALU register to register operations. When the CU detects an instruction that belongs to an R-type, it immediately goes to watch the FUNCTION field. At this point, according to its internal LUT, it sets properly the Control Word and the ALU op-code.

In order to have a better view on modelsim, we also set a variable IR, that holds the name of the instruction that is processed. A little abstract of the code is reported here:

Listing 3.2: R TYPE operation

```

case conv_integer(unsigned(IR_OPCODE)) is
2   when conv_integer(unsigned(RTYPE)) =>
        case conv_integer(unsigned(IR_FUNC)) is — if RTYPE instruction then watch
            function code
4             when conv_integer(unsigned(RTYPE.ADD)) =>
                    CW <= CW.RTYPE.ADD;
                    aluOpCod <= ADDop; — only for a clear view on modelsim
                    IR <= addr; — only for a clear view on modelsim
6             when conv_integer(unsigned(RTYPE.AND)) =>
                    CW <= CW.RTYPE.AND;
                    aluOpCod <= ANDop;
                    IR <= andr;
8             when conv_integer(unsigned(RTYPE.OR)) =>
                    CW <= CW.RTYPE.OR;
                    aluOpCod <= ORop;
                    IR <= orr;
10            . . .
12            . . .
14            . . .
16            . . .

```

3.3 J-type instruction

They are normal jump instructions. In our case we have both absolute and relative jump instructions. The procedure is the same that we use for the R-type instructions. The four jump types that the DLX can handle are reported here.

Listing 3.3: J-TYPE operation

```

when conv_integer(unsigned(JTYPE.JABS)) =>
2   CW <= CW_JTYPE.JABS;
   Jump <= '1';
   Jump_In <= '1';
   aluOpCod <= ADDop;
   IR <= j;
4   when conv_integer(unsigned(JTYPE.JAL)) =>
   CW <= CW_JTYPE.JAL;
   Jump <= '1';
   Jump_In <= '1';
   aluOpCod <= ADDop;
   IR <= jal;
6   when conv_integer(unsigned(JTYPE.JR)) =>
   CW <= CW_JTYPE.JR;
   BranchInst <= '1';
   JumpR_In <= '1';
   JumpRInst <= '1';
   aluOpCod <= ADDop;
   IR <= jr;
8   when conv_integer(unsigned(JTYPE.JALR)) =>
   CW <= CW_JTYPE.JALR;
   BranchInst <= '1';
   JumpR_In <= '1';
   JumpRInst <= '1';
   aluOpCod <= ADDop;
   IR <= jalr;
10  . . .
12  . . .
14  . . .
16  . . .
18  . . .
20  . . .
22  . . .
24  . . .
26  . . .

```


3.4 I-type instruction

Normally they are load and store instructions, operations with immediates or conditional branches. The handle of the branches instructions is discussed in a dedicated section. The procedure is the same of the previous two cases as we can see here below.

Listing 3.4: I TYPE operation

```

1 when conv_integer(unsigned(ITYPE.ADDI)) =>
2     CW <= CW_ITYPE.ADDI;
3     aluOpCod <= ADDOp;
4     IR <= addi;
5
6 when conv_integer(unsigned(ITYPE.ANDI)) =>
7     CW <= CW_ITYPE.ANDI;
8     aluOpCod <= ANDOp;
9     IR <= andi;
10
11 when conv_integer(unsigned(ITYPE.BEQZ)) =>
12     BranchZ_In <= '1';
13     BranchInst <= '1';
14     CW <= CW_ITYPE.BEQZ;
15     aluOpCod <= ADDOp;
16     IR <= beqz;
17
18 . . .

```

3.5 Branch and Jump management

If the instruction read from the I RAM is either a branch or a jump, an internal signal is risen in the CU according to the different kind of instructions.

Listing 3.5: Branch detection

```

1 when conv_integer(unsigned(ITYPE.BEQZ)) =>
2     BranchZ_In <= '1';
3     BranchInst <= '1';
4     CW <= CW_ITYPE.BEQZ;
5     aluOpCod <= ADDOp;
6     IR <= beqz;
7
8 when conv_integer(unsigned(ITYPE.BNEQZ)) =>
9     BranchNZ_In <= '1';
10    BranchInst <= '1';
11    CW <= CW_ITYPE.BNEQZ;
12    aluOpCod <= ADDOp;
13    IR <= bnez;

```

If the previously one was a **J**, **JAL**, the CU, through the jump signal, will change the input address of the I RAM, so the next instruction will not be the one located at the next sequential address, but the one situated at the address determined thanks to the **BrancAdd**. In this way we can fetch the right instruction without losing 1 clock cycle.

Instead for the other kind of branch and jump, the procedure is more complicated because we have to read the data from RF without affecting the execution of the previous instructions. In order to do that we have to wait until the decode phase in which the access to RF is performed. At this point for the branch we are able to determine if it will happen or not. Due to this delay, in case of taken branch, we will always execute a wrong instruction fetch and consequently we will lose 1 clock cycle. The same thing happens with **JR**, **JALR** because we have to read from the RF the branch address. To avoid that a wrong fetched instruction affects the state of the processor, a FLUSH operation is performed on the pipeline through a proper signal.

Listing 3.6: FLUSH

```

1 if (Branch_In='1') then -- eliminate the effect of CW if branch occurs
2     CWSF <= (others => '0');
3     end if;
4     Branch_In <= '0';
5     BranchInst <= '0';
6     Jump <= '0';
7     JumpRInst <= '0';
8     Jump_In <= '0';
9     JumpR_In <= '0';
10    StoreInst <= '0';
11    LHInst <= '0';

```

There are also two dedicated bits of the control word whose aim is to determine if the branch will occur or not and, based on this decision, also correct the DLX program counter.

Listing 3.7: Jump and branch affection

```

1  —CW(37) and CW(38) are two bit of selection of a multiplexer that determine if the next
   instruction will be affected by a jump or a branch
2
3  if (JumpR_In='1') then
4      CW(38) <= '0';
5      CW(37) <= '1';
6      JumpR_In <= '0';
7      JumpRInst <= '0';
8      BranchInst <= '0';
9  end if;
10
11 if (BranchZ_In='1') then
12     CW(38) <= '1';
13     CW(37) <= '0';
14     BranchZ_In <= '0';
15     BranchInst <= '0';
16 end if;
17
18 if (BranchNZ_In='1') then
19     CW(38) <= '1';
20     CW(37) <= '1';
21     BranchNZ_In <= '0';
22     BranchInst <= '0';
23 end if;


```

We decided to manage these operations in this way because is quiet simple and intuitive and also because is easier to test. 42 bits for the control word are a lot, but allow us to have under constant control the general situation during the test phase.

Data Path

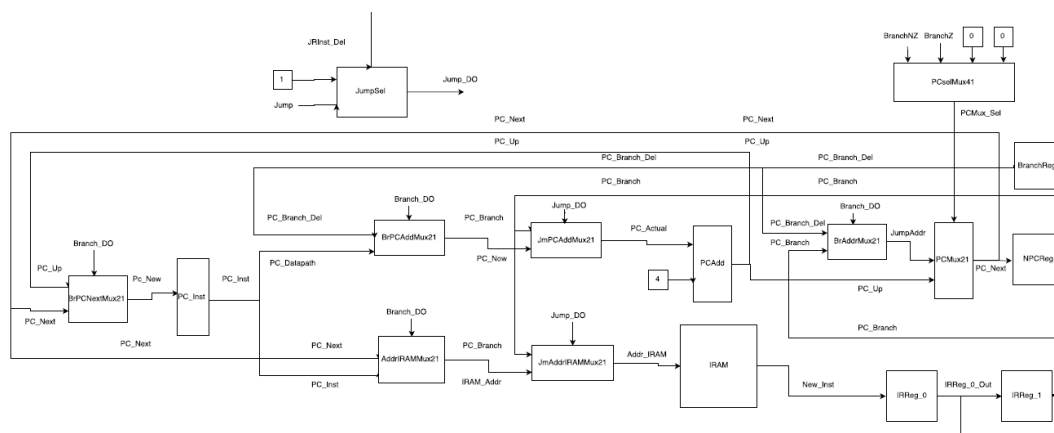4.1 Fetch

In this phase also the program counter is updated. The PCadd always adds 4 because we work with 32 bits instructions with memory width of 8 bits.



4.2 Decode

- **RF_AddrR1** read address for port 1 or RF
- **RF_AddrR2** read address for port 2 or RF
- **RF_AddrR3** write port RF address
- **ImmediateJ** target jump address
- **ImmediateI** immediate operand for I-type instruction

There are 5 output registers listed here below:

- **PCRetReg** stores return address for JAL and JALR
- **Areg** stores RF output form port1
- **Breg** stores RF output from port2
- **ImmReg** stores the extended operand (32 bits) for I-type instructions
- **RFWRAddrID** stores the write address for the current operation

In this stage is also present the logic used to determine, in case of branch instruction, if it has to be taken or not. This information is sent back to the previous stage so in the next clock cycle we know if we have to flush or not the pipeline.

4.2.1 Register file

The most important part of this stage is the register file, where all the data are stored. To handle the particular case in which we want both to write and read the same memory location, we decided to give the priority to the write phase, and the data that is being written in the memory is also reported to the output ready to be read. This allows us to remove some glitches and in this very particular case to save 1 clock cycle.

In the following abstract of code this mechanism is shown:

Listing 4.1: Register file

```

1 IF (CLK'EVENT AND CLK = '1') THEN
2     IF (ENABLE = '1') THEN
3         IF (WR = '1') THEN
4             REGISTERS(to_integer(unsigned(ADD.WR))) <= DATAIN;
5             —SIMULTANEOU R/W
6             IF ADD.WR = ADD.RD1 THEN
7                 OUT1 <= DATAIN;
8             END IF;
9             IF ADD.WR = ADD.RD2 THEN
10                OUT2 <= DATAIN;
11            END IF;
12        END IF;
13    ELSE —WHEN ENABLE '0' HIGH IMPEDANCE
14        OUT1 <= (OTHERS => 'Z');
15        OUT2 <= (OTHERS => 'Z');
16    END IF;
END IF;
```

4.3 Execute

In this stage all the operations on the data take place. There are three registers:

- **StatusRegEx** stores the status information of the previous ALU operation
- **ALUReg** stores the ALU output
- **DMEMAddrReg** depending on the instruction type, it can contains the data to be stored in the next mem stage

The StatusMux81 is a 8 to 1 multiplexer whose task is to select which ALU flag we want to save in the RF (greater, equal, lower, ...).

The ALU is in charge to perform all the computation that are needed on the data, according to the ALUop signals sent by the CU. It has two inputs and one output for the data and it is composed by five components: Multiplier, Adder-Subtractor, Shifter, Comparator and Logic unit.

4.3.1 ADDER

Our adder-subtractor is based on the P4 adder, this architecture allows to reduce the carry propagation delay which is the bottleneck in these kind of structures.

The P4 adder is based on two substructures as shown in 4.2, a carry generator and a sum generator.

 


Figure 4.2: P4 structure

The first one is the **sparse tree** that has to generate all the carries for the final computation of the sum. Its structure is a quiet particular and to obtain it we need two "elementary" blocks:

- **G** block that produces the following output: $G_{i:j} = G_{i:k} + P_{i:k} * G_{k-1:j}$
- **PG** has two outputs: one is the same of G and the other one is $P_{i:j} = P_{i:k} * P_{k-1:j}$

The tree structure is shown in 4.3. As we can see it is not properly linear and the VHDL code is not so simple to understand at a first view. It consists of 4 cycles, one for the first row (0), one for the two consequent (1 and 2), a third one for the third and the last one for all the consequents rows. In our case the depth is 5. The full code is reported in Appendix C.

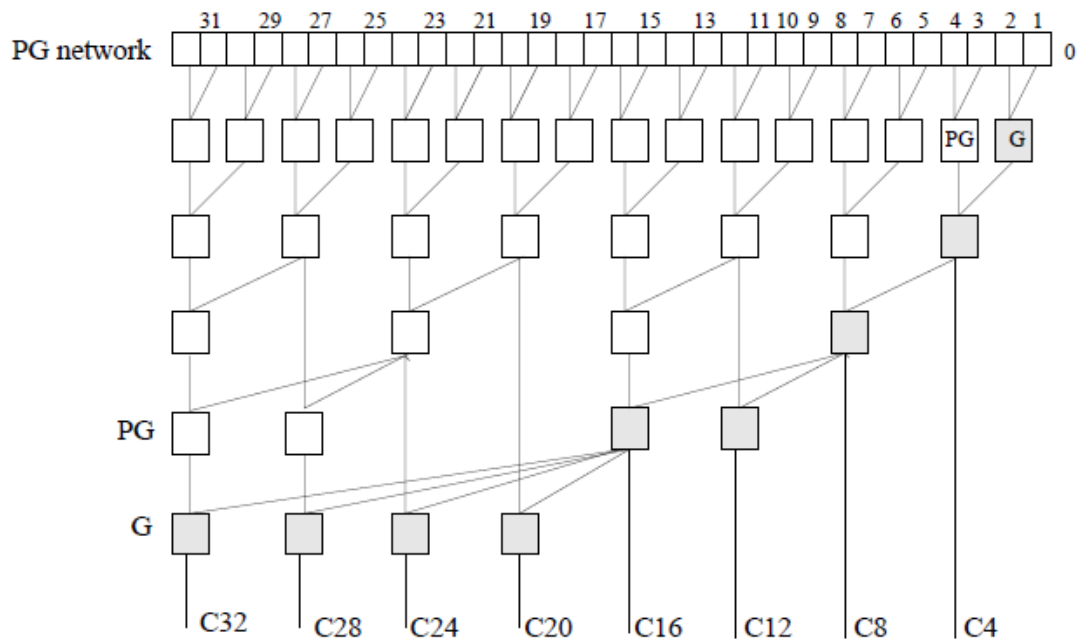


Figure 4.3: P4 carry tree structure

The structure of the top right PG was slightly modified in order to introduce the carry in and this permits both addition and subtraction.

The following part of the structure is the **carry select adder**. It is composed by several `carry_select_blocks` which generate 4 bits each one, by means of a small RCA supposing the input carry value. The component computes the result both for **carry-in = 0** and **carry-in = 1**. When the real one arrives from the above stage, a multiplexer chooses the right one. The structure of this stage is presented here. In this way the sum generation and the carry generation phases occurs at the same time and so the speed is increased.

 


Figure 4.4: P4 Adder: carry select adders

4.3.2 COMPARATOR

The comparator gives us the relationship between the two input, in both signed and unsigned cases. In order to manage this feature we use an additional signal that tells us how to manage the two data. The other inputs are the difference between the two operands and their MSBs. The logic is purely combinatorial and it works as follows:

Listing 4.2: Comparator

```

1 Temp(0) <= Diff (0);
3 Temp-g: for i in 1 to (Nbit-1) generate
    Temp(i) <= Temp(i-1) or Diff(i);
5 end generate;

7 Z <= not Temp(Nbit-1);
  sign_cntrl <= (signA xor signB) and (not unsign);
9 AgB <= (Carry and (not Z)) xor sign_cntrl;
  AgeqB <= Carry xor sign_cntrl;
11 AlB <= (not Carry) xor sign_cntrl;
  AleqB <= ((not Carry) or (Z)) xor sign_cntrl;
13 AeqB <= Z;
  AnoteqB <= not Z;

```

4.3.3 MULTIPLIER

We have implemented a multiplier based on the Wallace tree architecture shown in the figure 4.5. At the end of the tree an adder is necessary to obtain the final value. These choices have been made to improve the performance because this architecture is one of the fastest. The Carry Save Adders are normal adders, one of the fastest type, with 3 inputs and 2 outputs (sum and carry).

The VHDL code for this structure is just the mapping of the tree.

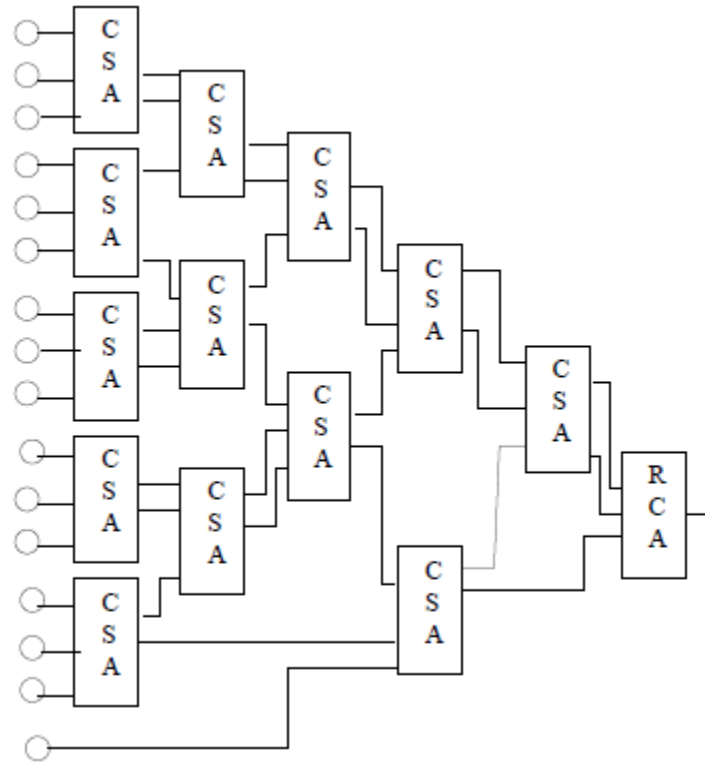


Figure 4.5: Wallace multiplier structure

This component is able to handle signed operands, this is done thanks to a logic that is present before the multiplier. It detects the signs of the operands and prepare them for the multiplication.

The following piece of code shows how we decide to handle it.

Listing 4.3: Sign handle

```

process(a, b, a_i, b_i)
2   begin
3       if ((a(Nbit/2-1) = '1') and (b(Nbit/2-1) = '1')) then
4           a_i <= std_logic_vector(unsigned(not(a)) + 1);
5           b_i <= std_logic_vector(unsigned(not(b)) + 1);
6       else
7           if (b(Nbit/2-1) = '1' and (a(Nbit/2-1) = '0')) then
8               a_i <= b;
9               b_i <= a;
10          else
11              a_i <= a;
12              b_i <= b;
13          end if;
14      end if;
15      for l in 0 to Nbit/2-1 loop
16          if (b_i(l) = '1') then
17              init(l)(Nbit/2-1+l downto l) <= a_i;
18              if (a_i(Nbit/2-1) = '1') then
19                  init(l)(Nbit-1 downto Nbit/2+l) <= (others=>'1');
20              else
21                  init(l)(Nbit-1 downto Nbit/2+l) <= (others=>'0');
22              end if;
23          else
24              init(l) <= zero;
25          end if;
26      end loop;
27  end process;

```

```

26 |         end loop;
    |     end process;

```

In order to avoid the overflow, we multiply only the lower 16 bits of the two operands. In this way we are sure that the result will always fit in 32 bits.

4.3.4 Shifter

Our choice for the shifter was not to use the T2 one, but another version. The main reason is that we wanted a circuit on one single stadio instead of three with a logic upstream, able to recognize all the possible scenarios with shift and rotate operations. In particular this is able to handle:

- Rotate left
- Rotate right
- Shift arithmetic left
- Shift arithmetic right
- Shift logic left
- Shift logic right

The implementation is very simple but very fast, it consists of a series of multiplexer 32 to 1 where each input corresponds to one of the bit that must be shifted. In this way by properly setting the selector of the mpx we are able to rotate all the 32 bits. If we want a shift, the logic upstream masks the undesired bits according to logical or arithmetic (the sign is maintained). The logic is also able to detect if there is a shift or a rotate for more than half of the number of bits (e.g. SLL 22). In this case it reverses the rotation to a right shift of 10 and the result is the same. In Appendix C the VHDL code for both the component and the logic are presented.

4.3.5 Logic unit

Also in this case we decide not to use the T2 logic (2 level) and we made our own logic unit component that is able to perform the same tasks with only one level of depth. As consequence of this the area is increased but the latency is decreased. The unit computes this 7 typologies of bitwise operations:

- NOT
- AND
- OR
- XOR
- NAND
- NOR
- XNOR

Also in this case the implementation is quiet simple, we use the fundamental logic gates to perform the tasks. An extract of the code is shown here below.

Listing 4.4: Logic unit

```

1 notAf:      for i in 0 to (Nbit-1) generate
2              notA(i) <= not A(i);
3              end generate;
5 notBf:      for i in 0 to (Nbit-1) generate
6              notB(i) <= not B(i);
7              end generate;
9 AandBf:     for i in 0 to (Nbit-1) generate

```



```

11         AandB(i) <= A(i) and B(i);
12         end generate;
13 Aorf:      for i in 0 to (Nbit-1) generate
14             AorB(i) <= A(i) or B(i);
15         end generate;
17 AxorBf:   for i in 0 to (Nbit-1) generate
18             AxorB(i) <= A(i) xor B(i);
19         end generate;
21 AnandBf:  for i in 0 to (Nbit-1) generate
22             AnandB(i) <= A(i) nand B(i);
23         end generate;
25 AnorBf:   for i in 0 to (Nbit-1) generate
26             AnorB(i) <= A(i) nor B(i);
27         end generate;
29 AxnorBf:  for i in 0 to (Nbit-1) generate
30             AxnorB(i) <= A(i) xnor B(i);
31         end generate;

```

4.4 Memory

Load and Store operations are performed in this stage. It is possible to read and write in different size:

- Word - 32 bits
- Half word - 16 bits
- Byte - 8 bits

Before the **Data memory**, two multiplexers are used, one for the data and one for the address respectively. Those because the load and store operations are codified in different ways so is necessary to swap the operands according to the instruction to be performed.

At the end of the stage is also present a write-back register (**WBReg**) for those instructions that do not use the **Data memory**.

4.5 Write back

This last stage consists of a single multiplexer that, after choosing the right input, reports back the data to the **Register file**.


The possible inputs of the mpx are:

- **StatusRegMEM** - the output of the comparator
- **LMDReg** - the output of Data memory
- **WBReg** - the output of an ALU operation
- **0** - to put at 0 one location of the RF

Simulation

The software used for the simulation is Modelsim, distributed by Altera. All the simulations are functional, so the delays of the signals are not take into account. To make the simulation phase easier and faster to understand, some internal meaningful signals were added to the waveform window and a script is used for the compilation. The final version of it is attached in Appendix D.

 
In Figure 5.1 is possible to see the behavior of the Register File when read and write commands occur. As we can see the output is available only when the enable signal is '1'.



In order to simulate a common use of our DLX, we wrote three test programs to show the main features of the microprocessor.

- The second one is explained here below.

16

 

CHAPTER 6

Synthesis

The tool used for the synthesis is design_vision, working in Synopsys environment. Also in this case some scripts were used in order to speed up the process. After a first synthesis, we tried to optimize the structure of the DLX both from timing and power point of view.

The top view structure of the component can be seen below, it consists of datapath and CU.

 


Figure 6.1: Structure of the DLX

To reduce the synthesis efforts, the memories were not synthesized. As we can see all the control signals start from the CU and go to the datapath.

6.1 ALU synthesis

For the DLX we create two different types of ALU named ALUv1 and ALUv2. The two have almost the same architecture and they are built with the same macro-components (multiplier, adder-subtractor, etc...). The main difference between the two typologies is in how the operands are provided to them and how the result is computed. In ALUv1 the operations run in parallel so for each new set of inputs we compute the addition, the multiplication, etc.. Because the operands A and B are directly provided to each one of the macro-components. The output then is selected through a mpx which selector is the ALUsel signal. This type of architecture is very fast but has the main disadvantage to be very power consuming due to the high switching activity. Instead in ALUv2 we add a preliminary stage in which we prepare the input for the macro-components. In this phase a process identifies through the ALUsel signal which operation must be preformed and according to this it sets the enable signal for that component.

Listing 6.1: ALUv2 enable signal generation

```

1 inputgenMUL:   for i in 0 to (Nbit/2-1) generate
2                 AinMUL(i) <= A(i) and enMUL;
3                 BinMUL(i) <= B(i) and enMUL;
4             end generate;
5
6 inputgen:      for i in 0 to (Nbit-1) generate
7                 AinADDSUB(i) <= A(i) and enADDSUB;
8                 BinADDSUB(i) <= B(i) and enADDSUB;
9                 AinSHIFTER(i) <= A(i) and enSHIFTER;
10                BinSHIFTER(i) <= B(i) and enSHIFTER;
11                AinLOGIC(i) <= A(i) and enLOGIC;
12                BinLOGIC(i) <= B(i) and enLOGIC;
13            end generate;
14
15 OUTgen: process (A,B,ALUsel,ADDSUBout,sumnsub,SHIFTERout,MULout,notAout,notBout,AandBout,
16                AorBout,AxorBout,AnandBout,AnorBout,AxnorBout)
17 begin
18     case (conv_integer(unsigned(ALUsel))) is
19         when (conv_integer(unsigned(ADDcode))) =>
20             ALUout <= ADDSUBout;
21             sumnsub <= '0';
22             enADDSUB <= '1';
23             enMUL <= '0';
24             enLOGIC <= '0';
25             enSHIFTER <= '0';
26             Shift_Rotaten <= '0';
27             Right_LeftN <= '0';
28         when (conv_integer(unsigned(SUBcode))) =>
29             ALUout <= ADDSUBout;
30             sumnsub <= '1';
31             enADDSUB <= '1';
32             enMUL <= '0';
33             enLOGIC <= '0';
34             enSHIFTER <= '0';
35             Shift_Rotaten <= '0';
36             Right_LeftN <= '0';
37         when (conv_integer(unsigned(MULcode))) =>
38             ALUout <= MULout;
39             enADDSUB <= '0';
40             enMUL <= '1';
41             enLOGIC <= '0';
42             enSHIFTER <= '0';
43             Shift_Rotaten <= '0';
44             Right_LeftN <= '0';

```

Then each input of the macroblock is putted in a bitwise AND with the proper enable signal. In this way for each new operation we will have only one pair of non-zero inputs and so only one macro-component will work at a given time. Finally the right result is selected through a mpx and displayed to the output. Thanks to this architecture it is possible to reduce the switching activity and so the overall power consumption of the ALU. The main drawback is the insertion of the AND gates that increase the critical path of the circuit as well as the area. These are the synthesis power reports for the two architectures:

```

*****
Report : power
        -analysis_effort low
Design : ALU_v2
Version: Z-2007.03-SP1
Date   : Thu Oct 19 00:19:24 2017
*****

```

Library(s) Used:

NangateOpenCellLibrary (File: /home/mariagrazia.graziano/do/libnangate/NangateOpenCellLibrary

Operating Conditions: typical Library: NangateOpenCellLibrary
Wire Load Model Mode: top

Design Wire Load Model Library

```
-----
ALU_v2                5K_hvratio_1_1    NangateOpenCellLibrary
```

Global Operating Voltage = 1.1

Power-specific unit information :

Voltage Units = 1V

Capacitance Units = 1.000000ff

Time Units = 1ns

Dynamic Power Units = 1uW (derived from V,C,T units)

Leakage Power Units = 1nW

Cell Internal Power = 1.6058 mW (46%)

Net Switching Power = 1.8933 mW (54%)

```
-----
Total Dynamic Power    = 3.4992 mW (100%)
```

Cell Leakage Power = 97.0791 uW

Report : power

-analysis_effort low

Design : ALU_v1_Nbit32

Version: Z-2007.03-SP1

Date : Thu Oct 19 01:05:12 2017

Library(s) Used:

NangateOpenCellLibrary (File: /home/mariagrazia.graziano/do/libnangate/NangateOpenCellLibrary)

Operating Conditions: typical Library: NangateOpenCellLibrary

Wire Load Model Mode: top

```
Design          Wire Load Model          Library
-----
```

```
ALU_v1_Nbit32    5K_hvratio_1_1    NangateOpenCellLibrary
```

Global Operating Voltage = 1.1

Power-specific unit information :

Voltage Units = 1V

Capacitance Units = 1.000000ff

Time Units = 1ns

Dynamic Power Units = 1uW (derived from V,C,T units)

Leakage Power Units = 1nW

Cell Internal Power = 6.4383 mW (52%)

Net Switching Power = 5.8908 mW (48%)

```
-----
Total Dynamic Power    = 12.3291 mW (100%)
```

Cell Leakage Power = 103.2780 uW

As we can see the ALUv1 consumes much more with respect to the ALUv2. For this reason the last one has been implemented in the final architecture of the DLX. In term of area and time there isn't a significant difference between the two versions.

6.2 DLX synthesis

The final script that we used is attached here and then commented step by step. After this we have further tried to improve the DLX in terms of power and area. The final results are displayed in the last part of this section.

Listing 6.2: Final synthesis script

```

1 analyze -library WORK -format vhdl {000-global.vhd}
2 analyze -library WORK -format vhdl {001-functions.vhd}
3 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-iv.vhd}
4 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-b-nd2.vhd}
5 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-c-mux21.vhd}
6 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-d-mux21N.vhd}
7 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-e-fa.vhd}
8 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-f-rcaN.vhd}
9 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-g-PGblock.vhd}
10 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-h-G.vhd}
11 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-i-PG.vhd}
12 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-l-
   SparseTreeCarryGenN.vhd}
13 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-m-CSBlockN.vhd}
14 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-n-CarrySumN.vhd}
15 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-o-AddSubN.vhd}
16 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-p-
   SparseTreeCarryGenNBM.vhd}
17 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-q-CSBlockNBM.vhd}
18 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-r-CarrySumNBM.vhd}
19 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-s-P4adderN.vhd}
20 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-t-CSA.vhd}
21 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-u-BoothMulWallace
   .vhd}
22 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-v-Comp.vhd}
23 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a-z-LogicFun_v2.vhd}
24 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a.za-Mux2to1.vhd}
25 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a.zb-mux32to1.vhd}
26 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a.zc-
   bidir_shift_rot_N.vhd}
27 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU.core/a.b.a.zd-
   bidir_shift_rot_N_interface.vhd}
28 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.a-ALU_v2.vhd}
29
30 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.c-fd_en.vhd}
31 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.d-LatchEn.vhd}
32 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.e-RegEn.vhd}
33
34 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.h-mux41.vhd}
35 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.i-mux41N.vhd}
36 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.l-mux81.vhd}
37 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.m-mux81N.vhd}
38 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.n-mux161N.vhd}
39
40 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.p-PC.vhd}
41
42
43 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.q-registerfile.vhd}
44
45 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.r-signExtension.vhd}
46
47 analyze -library WORK -format vhdl {a.b-Datapath.core/a.b.s-zeroTest.vhd}
48
49 analyze -library WORK -format vhdl {a.b-datapath.vhd}
50
51 analyze -library WORK -format vhdl {a.a-CU.HW.vhd}
52
53 analyze -library WORK -format vhdl {a-DLX.vhd}
54
55 elaborate DLX -architecture Structure
56
57 create_clock -name "Clk" -period 2.97 Clk
58
59 compile -map_effort high
60
61 report_timing > Report_DLX_time_opt_time.txt

```

```

63 report_power > Report_DLX_time_opt_pow.txt
63 report_area > Report_DLX_time_opt_area.txt

65 write -hierarchy -format ddc -output DLX-structural-time-opt.ddc

67 create_clock -name "Clk" -period 3.5 Clk

69 compile -map_effort high -power_effort high

71 report_timing > Report_DLX_pow_time_opt_time.txt
71 report_power > Report_DLX_pow_time_opt_pow.txt
73 report_area > Report_DLX_pow_time_opt_area.txt

75 write -hierarchy -format ddc -output DLX-structural-time-pow-opt.ddc

```

After created the needed folder, we analyzed the VHDL files and we elaborated the whole structure of the micorprocessor. In the next step we created a clock signal and compiled the DLX architecture. Then we extracted timing, area and power reports. After this we generated a constraint for the clock period and we compiled again with high map effort. For the power optimization phase we reduced the constraint for the clock and we compiled again with high power effort option.

These are the final results obtained with slack met condition. The first one shows the power report with only time optimization.

Design	Wire Load Model	Library
DLX	5K_hvratio_1_1	NangateOpenCellLibrary

```

Global Operating Voltage = 1.1
Power-specific unit information :
  Voltage Units = 1V
  Capacitance Units = 1.000000ff
  Time Units = 1ns
  Dynamic Power Units = 1uW      (derived from V,C,T units)
  Leakage Power Units = 1nW

```

```

Cell Internal Power   =   4.8464 mW   (86%)
Net Switching Power  =  787.4512 uW   (14%)
-----
Total Dynamic Power   =   5.6338 mW   (100%)

Cell Leakage Power    =  474.8714 uW

```

After some attempts, the minimum clock period achived is 2,97 ns and so the maximum working clock frequency is: 336,7 MHz.

The second one shows the power dissipation with both time and power optimization. In this case we are able to save about 14% of the power, but the maximum clock frequency is consequently decreased of about the same percentage. The maximum achieved clock frequency in this case is 289,86 MHz.

Design	Wire Load Model	Library
DLX	5K_hvratio_1_1	NangateOpenCellLibrary

Global Operating Voltage = 1.1

Power-specific unit information :

Voltage Units = 1V

Capacitance Units = 1.000000ff

Time Units = 1ns

Dynamic Power Units = 1uW (derived from V,C,T units)

Leakage Power Units = 1nW

Cell Internal Power = 4.1560 mW (86%)

Net Switching Power = 678.8270 uW (14%)

Total Dynamic Power = 4.8349 mW (100%)

Cell Leakage Power = 469.9623 uW

CHAPTER 7

Place & Routing

The last step to be performed was the physical design implementation of our DLX using Encounter. We started by adding the power rings, stripes and cell placement. Then we performed the clock tree synthesis and also the routing. During geometry check we had no violations. The gate count report was extracted and here are some of the information it provides:

Module	Gates	Cells	Area μm^2
DLX	25467	11744	20322,7
Datapath	23875	11181	19052,2
ALU	5206	3606	4154,4
MUL	3458	2326	2759,5
CU	1515	507	1209,5

 


Figure 7.1: DLX ameoba view

APPENDIX A

Instructions

A.1 Instruction set

add	
jalr	
addi	jr
and	lb
andi	lbu
beqz	lhi
bnez	lhu
j	sb
jal	seq
lw	seqi
nop	sgeu
or	sgeui
ori	sgt
sge	sgti
sgei	sgtu
sle	sgtui
slei	slt
sll	slti
slli	sltu
sne	sltui
snei	sra
srl	srai
srli	subu
sub	subui
subi	mult
sw	rol
xor	ror
xori	roli
addu	rori
addui	

The explanation of each instruction is reported in the DLX project guide.

APPENDIX B

Datapath

B.1 Structure

 


Figure B.1: Datapath structure

APPENDIX C

VHDL

C.1 SparseTreeCarryGenN

```
LIBRARY IEEE;
USE IEEE.std_logic_1164.all;
USE WORK.functions.all;

ENTITY SparseTreeCarryGenN IS
  GENERIC ( Nbit: integer:=16 );
  PORT (
    A :      IN std_logic_vector (Nbit-1 downto 0);
    B :      IN std_logic_vector (Nbit-1 downto 0);
    Cin :    IN std_logic;
    Cout :   OUT std_logic_vector ((Nbit/4) downto 0));
END SparseTreeCarryGenN;

ARCHITECTURE Structure OF SparseTreeCarryGenN IS

  TYPE SignalVector IS ARRAY (log2_N(Nbit) DOWNTO 0) OF std_logic_vector(1 to Nbit);
  SIGNAL prop : SignalVector;
  SIGNAL gen : SignalVector;
  SIGNAL propcin: std_logic;
  SIGNAL gencin: std_logic;

  COMPONENT G IS
    PORT (
      G1:      IN std_logic;
      P1:      IN std_logic;
      G2:      IN std_logic;
      Gout:     OUT std_logic);
  END COMPONENT;

  COMPONENT PG IS
    PORT (
      G1:      IN std_logic;
      P1:      IN std_logic;
      G2:      IN std_logic;
      P2:      IN std_logic;
      Gout:     OUT std_logic;
      Pout:     OUT std_logic);
  END COMPONENT;

  COMPONENT PGblock IS
    PORT (
      A :      IN std_logic;
      B :      IN std_logic;
      G :      OUT std_logic;
      P :      OUT std_logic);
  END COMPONENT;

  BEGIN

  rowgen: FOR row IN 0 TO log2_N(Nbit) GENERATE
    row0: IF row=0 GENERATE
      e10: FOR I IN 1 TO Nbit GENERATE
        cin_prop: IF ( I=1 ) GENERATE
          Cinprop: PGblock PORT MAP ( A(i-1), B(i-1), gencin ,
            propcin);
          gen(row)(i) <= (gencin OR (propcin AND Cin));
        END GENERATE;
        other_prop: IF (I>1) GENERATE
          PGb: PGblock PORT MAP ( A(i-1), B(i-1), gen(row)(i),
            prop(row)(i));
        END GENERATE;
      END GENERATE;
    END GENERATE;

    row1_2: IF row < 3 and row /= 0 GENERATE
```

```

row1_2:FOR I IN 1 TO Nbit/2**row GENERATE
  G_12: IF I=1 GENERATE
    G1_2: G PORT MAP (gen(row-1)(2**(row)),prop(row-1)(2**(row)),gen(row-1)(2**(row)-row),gen(row)(2**row));
  END GENERATE;
  PG_12: IF I>1 GENERATE
    PG1_2: PG PORT MAP (gen(row-1)(i*2**row),prop(row-1)(i*2**row),gen(row-1)(i*2**row)-2**(row-1),prop(row-1)(i*2**row)-2**(row-1),gen(row)(i*2**row),prop(row)(i*2**row));
  END GENERATE;
END GENERATE;
END GENERATE;

row3: IF row = 3 GENERATE
  e13:FOR I IN 1 TO Nbit/4 GENERATE
    W_3: IF (I mod 2)=1 GENERATE
      gen(row)(i*2**row-1) <= gen(row-1)(i*2**row-1);
      prop(row)(i*2**row-1) <= prop(row-1)(i*2**row-1);
    END GENERATE;
    G_3: IF (I=2) GENERATE
      G3: G PORT MAP (gen(row-1)(i*2**row-1),prop(row-1)(i*2**row-1),gen(row-1)(i*2**row-1)-2**(row-1),gen(row)(i*2**row-1));
    END GENERATE;
    PG_3: IF ((I mod 2)=0 and (I > 2)) GENERATE
      PG3: PG PORT MAP (gen(row-1)(i*2**row-1),prop(row-1)(i*2**row-1),gen(row-1)(i*2**row-1)-2**(row-1),prop(row-1)(i*2**row-1)-2**(row-1),gen(row)(i*2**row-1),prop(row)(i*2**row-1));
    END GENERATE;
  END GENERATE;
END GENERATE;

row3e: IF row > 3 GENERATE
  e13_e:FOR I IN 0 TO Nbit/4-1 GENERATE
    W_3e: IF ((I rem (2**(row-2)))<((2**(row-2))/2)) GENERATE
      gen(row)((i+1)*4) <= gen(row-1)((i+1)*4);
      prop(row)((i+1)*4) <= prop(row-1)((i+1)*4);
    END GENERATE;
    G_3e: IF (((I rem (2**(row-2)))>=((2**(row-2))/2)) and (I < 2**(row-2))) GENERATE
      G3_E: G PORT MAP (gen(row-1)((i+1)*4),prop(row-1)((i+1)*4),gen(row-1)((i+1)*4)-((i+1)-2**(row-3))*4,gen(row)((i+1)*4));
    END GENERATE;
    PG_3e: IF (((I rem (2**(row-2)))>=((2**(row-2))/2)) and (I > 2**(row-2))) GENERATE
      PG3_E: PG PORT MAP (gen(row-1)((i+1)*4),prop(row-1)((i+1)*4),gen(row-1)((i+1)*4)-((i+1)-2**(row-3)-4*(i/(2**(row-2)))*(2**(row-4))))*4,prop(row-1)((i+1)*4)-((i+1)-2**(row-3)-4*(i/(2**(row-2)))*(2**(row-4))))*4,gen(row)((i+1)*4),prop(row)((i+1)*4));
    END GENERATE;
  END GENERATE;
END GENERATE;
END GENERATE;

outgen: FOR I IN 0 TO Nbit GENERATE
  Cout_0: IF i=0 GENERATE
    Cout(0) <= Cin;
  END GENERATE;
  Cout_ot:IF (((i mod 4)=0) and (i /= 0)) GENERATE
    Cout(i/4) <= gen(log2_N(Nbit))(i);
  END GENERATE;
END GENERATE;

END Structure;

```

C.2 bidir_shift_rot_N_logic

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.numeric_std.all;
use work.global.all;
use work.functions.all;

ENTITY bidir_shift_rot_N_interface IS
generic (
  Nbit: integer := Nbit);
PORT (
  data_in      : IN STD_LOGIC_VECTOR(Nbit-1 downto 0);
  moves        : IN STD_LOGIC_VECTOR(log2_N(Nbit)-1 downto 0);
  tot          : IN STD_LOGIC;
  shift_rotN   : IN STD_LOGIC;
  right_leftN  : IN STD_LOGIC;
  arith_logN   : IN STD_LOGIC;
  data_out     : OUT STD_LOGIC_VECTOR(Nbit-1 downto 0));
END bidir_shift_rot_N_interface;

ARCHITECTURE struct OF bidir_shift_rot_N_interface IS

COMPONENT bidir_shift_rot_N IS
  generic (
    Nbit: integer := Nbit);
  PORT (
    data_in      : IN STD_LOGIC_VECTOR(Nbit-1 downto 0);
    sel          : IN STD_LOGIC_VECTOR(log2_N(Nbit)-1 downto 0);
    shift        : IN STD_LOGIC_VECTOR(Nbit-1 downto 0);
    dx           : IN STD_LOGIC;
    arith_logN   : IN STD_LOGIC;
    data_out     : OUT STD_LOGIC_VECTOR(Nbit-1 downto 0));
END COMPONENT;

signal move : integer range 0 to 16;
signal move0 : integer range 0 to 31;
signal selt   : std_logic_vector(log2_N(Nbit)-1 downto 0);
signal shiftt : std_logic_vector(Nbit-1 downto 0);
signal r_l    : std_logic;

BEGIN

move0 <= to_integer(unsigned(moves));

process(data_in, shift_rotN, right_leftN, move0)
begin
  if(right_leftN = '1') then
    if(move0 > 16) then
      move <= 32-move0;
      r_l <= '0';
    else
      move <= move0;
      r_l <= '1';
    end if;
  end if;
  if(right_leftN = '0') then
    if(move0 > 15) then
      move <= 32-move0;
      r_l <= '1';
    else
      move <= move0;
      r_l <= '0';
    end if;
  end if;
end process;

process(move, r_l)
begin
  if(r_l = '1') then
    case move is
      when 0 => selt <= "00000";
      when 1 => selt <= "00001";
      when 2 => selt <= "00010";
      when 3 => selt <= "00011";
      when 4 => selt <= "00100";
      when 5 => selt <= "00101";
      when 6 => selt <= "00110";
      when 7 => selt <= "00111";
      when 8 => selt <= "01000";
      when 9 => selt <= "01001";
      when 10 => selt <= "01010";
    end case;
  end if;
end process;

```

[illegible]


```

        end if;
        if (tot = '1' and shift_rotN = '1') then
            shiftt <= (others => '1');
        end if;
    else
        shiftt <= "00000000000000000000000000000000";
    end if;
end process;

bidir1: bidir_shift_rot_N PORT MAP (data_in, selt, shiftt, right_leftN,
    arith_logN, data_out);

END struct;

```

C.3 bidir_shift_rot_N

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_signed.all;
USE work.global.all;
USE work.functions.all;

ENTITY bidir_shift_rot_N IS
    generic (
        Nbit: integer := Nbit);
    PORT (
        data_in      : IN STD_LOGIC_VECTOR(Nbit-1 downto 0);
        sel          : IN STD_LOGIC_VECTOR(log2_N(Nbit)-1 downto 0);
        shift         : IN STD_LOGIC_VECTOR(Nbit-1 downto 0);
        dx           : IN STD_LOGIC;
        arith_logN    : IN STD_LOGIC;
        data_out      : OUT STD_LOGIC_VECTOR(Nbit-1 downto 0));
END bidir_shift_rot_N;

```

```

-- data_in      : 00000
-- right_rot1   : 00001
-- right_rot2   : 00010
-- right_rot3   : 00011
-- right_rot4   : 00100
-- right_rot5   : 00101
-- right_rot6   : 00110
-- right_rot7   : 00111
-- right_rot8   : 01000
-- right_rot9   : 01001
-- right_rot10  : 01010
-- right_rot11  : 01011
-- right_rot12  : 01100
-- right_rot13  : 01101
-- right_rot14  : 01110
-- right_rot15  : 01111
-- right_rot16  : 10000
-- left_rot1    : 10001
-- left_rot2    : 10010
-- left_rot3    : 10011
-- left_rot4    : 10100
-- left_rot5    : 10101
-- left_rot6    : 10110
-- left_rot7    : 10111
-- left_rot8    : 11000
-- left_rot9    : 11001
-- left_rot10   : 11010
-- left_rot11   : 11011
-- left_rot12   : 11100
-- left_rot13   : 11101
-- left_rot14   : 11110
-- left_rot15   : 11111

```

ARCHITECTURE struct OF bidir_shift_rot_N IS

```

    COMPONENT Mux2to1 IS
        PORT (
            x1 : IN STD_LOGIC;
            x2 : IN STD_LOGIC;
            s  : IN STD_LOGIC;
            f  : OUT STD_LOGIC);
    END COMPONENT;

```

```

    COMPONENT mux32to1 IS
        PORT (
            A0, A1, A2, A3, A4, A5, A6, A7 : IN STD_LOGIC;
            A8, A9, A10, A11, A12, A13, A14, A15 : IN STD_LOGIC;
            A16, A17, A18, A19, A20, A21, A22, A23 : IN STD_LOGIC;
            A24, A25, A26, A27, A28, A29, A30, A31 : IN STD_LOGIC;
            s : IN STD_LOGIC_VECTOR(5-1 downto 0);
            F : OUT STD_LOGIC);
    END COMPONENT;

```

```

END COMPONENT;

SIGNAL muxout: STD_LOGIC_VECTOR(Nbit-1 downto 0);
SIGNAL dffout_t: STD_LOGIC_VECTOR(2*Nbit-1 downto 0);
SIGNAL dffout_tt: STD_LOGIC_VECTOR(2*Nbit-1 downto 0);
SIGNAL U: STD_LOGIC_VECTOR(Nbit-1 downto 0);
SIGNAL data: STD_LOGIC;

BEGIN

    stages: FOR I IN Nbit/2 TO Nbit+Nbit/2-1 GENERATE

        muxes: mux32to1 PORT MAP (data_in(I-Nbit/2), dffout_tt(I+1), dffout_tt(I+2), dffout_tt(I+3), dffout_tt(I+4), dffout_tt(I+5), dffout_tt(I+6), dffout_tt(I+7), dffout_tt(I+8), dffout_tt(I+9), dffout_tt(I+10), dffout_tt(I+11), dffout_tt(I+12), dffout_tt(I+13), dffout_tt(I+14), dffout_tt(I+15), dffout_tt(I+16), dffout_tt(I-15), dffout_tt(I-14), dffout_tt(I-13), dffout_tt(I-12), dffout_tt(I-11), dffout_tt(I-10), dffout_tt(I-9), dffout_tt(I-8), dffout_tt(I-7), dffout_tt(I-6), dffout_tt(I-5), dffout_tt(I-4), dffout_tt(I-3), dffout_tt(I-2), dffout_tt(I-1), sel, muxout(I-Nbit/2));
        data <= data_in(Nbit-1) and dx and arith_logN;
        mpxs: Mux2to1 PORT MAP (muxout(I-Nbit/2), data, shift(I-Nbit/2), U(I-Nbit/2));
        dffout_t(I) <= data_in(I-Nbit/2);
    END GENERATE;
    dffout_tt(2*Nbit-1 downto Nbit+Nbit/2) <= dffout_t(Nbit-1 downto Nbit/2);
    dffout_tt(Nbit/2-1 downto 0) <= dffout_t(Nbit+Nbit/2-1 downto Nbit);
    dffout_tt(Nbit+Nbit/2-1 downto Nbit/2) <= dffout_t(Nbit+Nbit/2-1 downto Nbit/2);
    ;

    data_out <= U;

END struct;

```

APPENDIX D

SCRIPTS AND PROGRAMS

D.1 Final simulation script

```
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/000-global.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/001-functions.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.a-iv.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.b-nd2.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.c-mux21.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.d-mux21N.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.e-fa.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.f-rcaN.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.g-PGblock.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.h-G.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.i-PG.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.l-SparseTreeCarryGenN.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.m-CSBlockN.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.n-CarrySumN.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.o-AddSubN.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.p-SparseTreeCarryGenNBM.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.q-CSBlockNBM.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.r-CarrySumNBM.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.s-P4adderN.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.t-CSA.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.u-BoothMulWallace.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.v-Comp.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.z-LogicFun_v2.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.za-Mux2to1.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.zb-mux32to1.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.zc-bidir_shift_rot_N.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.core/a.b.a.zd-bidir_shift_rot_N_interface.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.a-ALU.v2.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.b-DataMemory.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.c-fd.en.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.d-LatchEn.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.core/a.b.e-RegEn.vhd
```

```

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.h-mux41.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.i-mux41N.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.l-mux81.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.m-mux81N.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.n-mux161N.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.o-IRAM.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.p-PC.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.q-registerfile.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.r-signExtension.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-Datapath.
core/a.b.s-zeroTest.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.b-datapath.
vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a.a-CUHW.vhd

vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/a-DLX.vhd
vcom -reportprogress 300 -work work /home/ms17.19/Project/DLX_final/sim/testbench/
tb_DLX.vhd

vsim -t 100ps -novopt work.tb_DLX(TEST)
add wave *
add wave sim:/tb_dlx/DUT/CU/*
add wave sim:/tb_dlx/DUT/datap/*
add wave sim:/tb_dlx/DUT/datap/RF/*
add wave sim:/tb_dlx/DUT/datap/ALU/*
add wave sim:/tb_dlx/DUT/datap/DataMem/*

```

D.2 4x4 matrix multiplication

```

addi r1,r0,#1 ;S11
addi r2,r0,#1 ;S12
addi r3,r0,#1 ;S13
addi r4,r0,#1 ;S14
addi r5,r0,#1 ;S21
addi r6,r0,#1 ;S22
addi r7,r0,#1 ;S23
addi r8,r0,#1 ;S24
addi r9,r0,#1 ;S31
addi r10,r0,#1 ;S32
addi r11,r0,#1 ;S33
addi r12,r0,#1 ;S34
addi r13,r0,#1 ;S41
addi r14,r0,#1 ;S42
addi r15,r0,#1 ;S43
addi r16,r0,#1 ;S44
sw 4(r0),r1 ; store S11
addi r17,r0,#1 ;S11
addi r18,r0,#1 ;S12
addi r19,r0,#1 ;S13
addi r20,r0,#1 ;S14
addi r21,r0,#1 ;S21
addi r22,r0,#1 ;S22
addi r23,r0,#1 ;S23
addi r24,r0,#1 ;S24
addi r25,r0,#1 ;S31
addi r26,r0,#1 ;S32
addi r27,r0,#1 ;S33
addi r28,r0,#1 ;S34
addi r29,r0,#1 ;S41
addi r30,r0,#1 ;S42
addi r31,r0,#1 ;S43
addi r1,r0,#1 ;S44
sw 8(r0),r2 ; store S12
sw 12(r0),r3 ; store S13
sw 16(r0),r4 ; store S14
sw 20(r0),r5 ; store S21
sw 24(r0),r6 ; store S22
sw 28(r0),r7 ; store S23
sw 32(r0),r8 ; store S24
sw 36(r0),r9 ; store S31
sw 40(r0),r10 ; store S32
sw 44(r0),r11 ; store S33
sw 48(r0),r12 ; store S34
sw 52(r0),r13 ; store S41
sw 56(r0),r14 ; store S42
sw 60(r0),r15 ; store S43
sw 64(r0),r16 ; store S44
sw 68(r0),r17 ; store S11
sw 72(r0),r18 ; store S12
sw 76(r0),r19 ; store S13
sw 80(r0),r20 ; store S14
sw 84(r0),r21 ; store S21
sw 88(r0),r22 ; store S22
sw 92(r0),r23 ; store S23
sw 96(r0),r24 ; store S24
sw 100(r0),r25 ; store S31
sw 104(r0),r26 ; store S32
sw 108(r0),r27 ; store S33
sw 112(r0),r28 ; store S34
sw 116(r0),r29 ; store S41
sw 120(r0),r30 ; store S42
sw 124(r0),r31 ; store S43
sw 128(r0),r1 ; store S44
addi r16,r0,#64 ;
addi r17,r0,#4 ; start address matrix 1
addi r10,r0,#0 ; reset accumulator
addi r31,r0,#4 ;number of row
addi r29,r0,#4 ;number of column
addi r20,r0,#160 ; memory start address for result matrix
addi r30,r0,#16 ;number of operations
addi r3,r0,#4 ; first address of matrix 1
addi r4,r0,#68 ; first address of matrix 2
addi r1,r0,#0
addi r2,r0,#0
nop
nop
mulsum:
lw r5,0(r3) ;load number of matrix 1
lw r6,0(r4) ;load number of matrix 2
subi r31,r31,#1 ;update counter of column

```

```
addi r3,r3,#4 ; update address row
addi r4,r4,#16 ; update column address
nop
nop
mult r7,r5,r6 ;product
nop
nop
nop
nop
nop
add r10,r10,r7 ; sum of product
bnez r31,mulsum
subi r29,r29,#1 ; update number of operation in row
subi r30,r30,#1 ; update number of calculation
addi r31,r0,#4 ; restore counter of column
subi r4,r4,#60 ; new column
nop
nop
nop
bnez r29,firstrow
addi r17,r17,#16 ; new row
addi r4,r0,#68 ; restore first address of matrix 2
addi r29,r0,#4 ;
nop
nop
nop
nop
firstrow:
add r3,r0,r17 ; new row start address
nop
sw 0(r20),r10 ; store result of multiplication 164 184 204 224
addi r20,r20,#4 ; update store address for result
addi r10,r0,#0 ; reset accumulator
nop
nop
bnez r30,mulsum
nop
nop
nop
nop
nop
nop
```